

Answer key and Marking Scheme

Answers	Marks
D. The voltage across the LC combination will remain the same.	1
C. 5 A	1
A. 1/6	1
A. Lower cost	1
D. 920	1
B. 3	1
B. B	1
A. Both A and R are true and R is the correct explanation of A	1
C. A is true but R is false	1
C. A is true but R is false	1
<p>(a) Yes. (0.5 marks)</p> <p>(b) No. (0.5 marks)</p> <p>(c) Since both the speakers are connected to an inductor, the current in an inductive circuit decreases with increasing frequency. Thus, an inductor connected in series with a speaker blocks high-frequency signals and allows low-frequency signals. So both speaker 1 and 2 will deliver low-frequency signals.</p> <p>(1 mark)</p> <p>Correction:</p> <p>If speaker 2 is connected to a capacitor instead of an inductor, the capacitor blocks low-frequency signals and passes high-frequency signals. This is because the current in a capacitive circuit increases with increasing frequency. So speaker 2 connected to a capacitor in series will deliver high-frequency signals, as desired.</p> <p>(1 mark)</p>	3
(a) Radio P will allow the person to hear the radio channel of frequency f_0 , without the interference of other frequencies. (0.5 marks)	3

<p>Both f_1 and f_2 do not lie in the bandwidth of the radio P while frequency f_1 lies in the bandwidth of radio Q. (0.5 marks)</p> <p>(b) The maximum current at resonance in an LCR circuit is given by</p> $i_{\max} = V/R$ <p>Since $i_P > i_Q$, the resistance of circuit used in radio P is less than the resistance of the circuit used in radio Q.</p> <p><i>(0.5 marks for correct answer and 0.5 marks for correct reason)</i></p> <p>The resonance frequency $f_0 = 1/(2\pi\sqrt{LC})$</p> <p>As L and f_0 is the same for both circuits the capacitance of both circuits will be the same.</p> <p><i>(0.5 marks for correct answer and 0.5 marks for correct reason.)</i></p>	
<p>a. For angular frequency $\nu = 50 \text{ Hz}$</p> <p>Inductive reactance $X_L = \omega L = 2\pi \times 50 \times 10 \times 10^{-3} = \pi \text{ ohm}$</p> $I_{\text{rms}} = V_{\text{rms}}/X_L = 100/\pi \text{ A}$ <p>[0.5 mark for correct value of I_{rms}]</p> <p>For angular frequency $\nu = 50 \text{ kHz}$</p> <p>Inductive reactance $X'_L = \omega L = 2\pi \times 50 \times 10^3 \times 10 \times 10^{-3} = 1000\pi \text{ ohm}$</p> $I'_{\text{rms}} = V_{\text{rms}}/X_L = 1/10\pi \text{ A}$ <p>[0.5 mark for correct value of I'_{rms}]</p> <p>% decrease in I_{rms}</p> $= \Delta I_{\text{rms}} / I_{\text{rms}} \times 100$ $= 999\pi / (10\pi \times 100) \times 100$ $= 99.9 \%$ <p>[1 mark for correct calculation of % decrease of I_{rms}]</p> <p>b. Bulb glows dimmer.</p> <p>[0.5 mark for correct conclusion]</p>	3

<p>Increase in angular frequency increases the inductive reactance that further results in the decrease in I_{rms} current flowing through the bulb. Hence the bulb glows dimmer.</p> <p>[0.5 mark for correct reason explanation]</p>	
<p>a. 100 ohm Resistor:</p> <p>Voltage across R = $10\sin 100\pi t$</p> <p>Current $i = V/R$</p> <p>$= 10\sin 100\pi t / 100$</p> <p>$= 0.1 \sin 100\pi t$</p> <p>[0.5 mark for voltage & 0.5 mark for correct expression of current]</p> <p>b. 10μF Capacitor:</p> <p>Voltage across C = $10\sin 100\pi t$</p> <p>Current $i = 10\sin 100\pi t / X_c$</p> <p>Here $X_c = 1/C\omega = 1000/\pi$ ohm</p> <p>Current through C = $i = V/X_c$</p> <p>$= 10\sin(100\pi t + \pi/2) / (1000/\pi)$</p> $= \frac{10 \sin \left(100\pi t + \frac{\pi}{2}\right)}{\left(\frac{1000}{\pi}\right)} = \frac{\pi}{100} \sin \left(100\pi t + \frac{\pi}{2}\right)$ <p>[0.5 mark for voltage & 1 mark for correct expression of current]</p> <p>c. 10mH Inductor :</p> <p>Voltage across L = $10\sin 100\pi t$</p> <p>Inductive reactance, $X_L = L\omega = 10 \times 10^{-3} \times 100\pi = \pi$ ohm</p> <p>Current through an inductor, $i = V/X_L$</p> $= \frac{10}{\pi} \sin \left(100\pi t - \frac{\pi}{2}\right)$ <p>[0.5 mark for voltage & 1 mark for correct expression of current]</p>	<p>4</p>
<p>In circuit (i):</p>	<p>3</p>

$$I = \frac{V}{Z} = \frac{V}{\sqrt{R^2 + \left(\frac{1}{C\omega}\right)^2}}$$

$$I/2 = \frac{V}{Z'} = \frac{V}{\sqrt{R^2 + \left(\frac{3}{C\omega}\right)^2}}$$

Substituting for I,

$$\frac{V}{\sqrt{R^2 + \left(\frac{1}{C\omega}\right)^2}} = \frac{2V}{\sqrt{R^2 + \left(\frac{3}{C\omega}\right)^2}}$$

[1 mark for expression for currents]

Transposing and solving:

$$3R^2 = 5 \left(\frac{1}{C\omega}\right)^2 = 5X_C^2$$

$$X_C/R = \sqrt{3}/\sqrt{5}$$

[0.5 mark for correct ratio X_C/R]

In circuit (ii):

$$I = \frac{V}{Z} = \frac{V}{\sqrt{R^2 + (L\omega)^2}}$$

$$2I = \frac{V}{Z} = \frac{V}{\sqrt{R^2 + L^2\omega^2/9}}$$

Substituting for I,

$$\frac{2V}{\sqrt{R^2 + (L\omega)^2}} = \frac{V}{\sqrt{R^2 + L^2\omega^2/9}}$$

[1 mark for expression for currents]

Transposing and solving,

$$X_L/R = 3\sqrt{3}/\sqrt{5}$$

So the ratio:

$$X_C / X_L = 1/3$$

[0.5 mark for correct final ratio]

